

Truth Table (A2)


Copyright (c) 2025-2011 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Truth Table

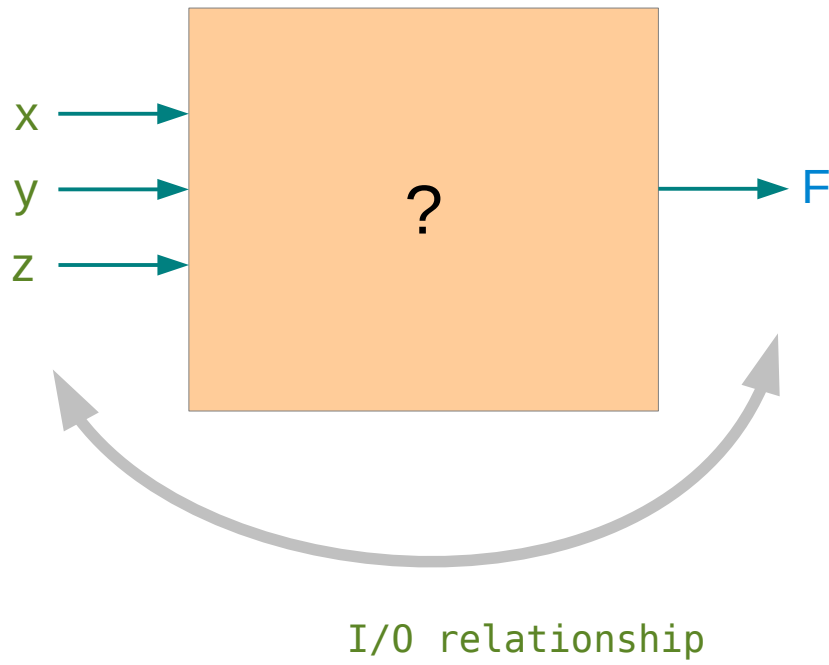


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

inputs output


Finding minterms and Maxterms

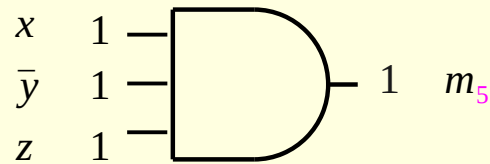Consider the case when $x=1$ and $y=0$ and $z=1$ index = 5



$$(x=1) \wedge (y=0) \wedge (z=1) \iff$$
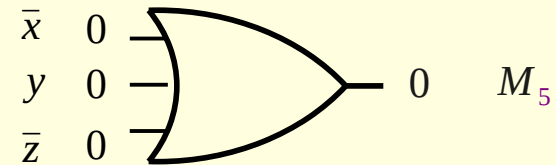
$$(x=1) \wedge (\bar{y}=1) \wedge (z=1) \iff m_5=1$$




$$(x=1) \wedge (y=0) \wedge (z=1) \iff$$

$$(\bar{x}=0) \wedge (y=0) \wedge (\bar{z}=0) \iff M_5=0$$

minterm m_5

index 5

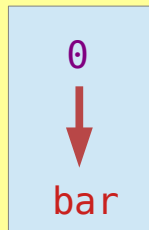


binary 101

$$x \cdot \bar{y} \cdot z = 1$$

Maxterm M_5


index 5

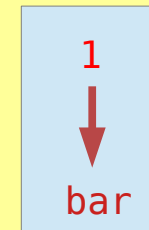


binary 101

$$\bar{x} + y + \bar{z} = 0$$

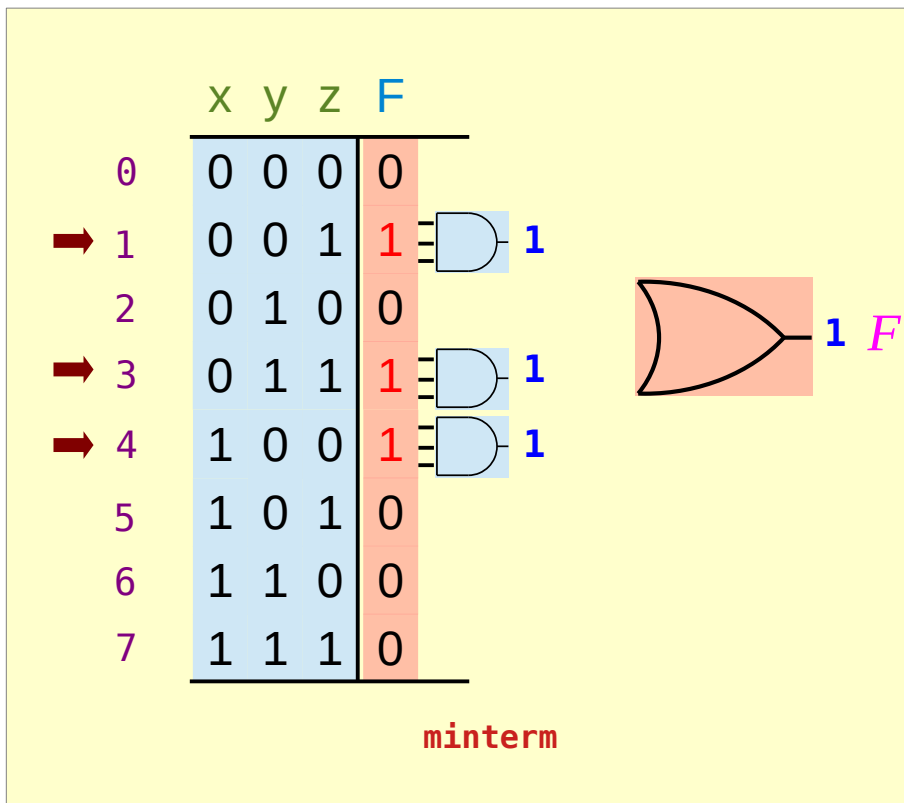Boolean Function **F** with minterms and Maxterms




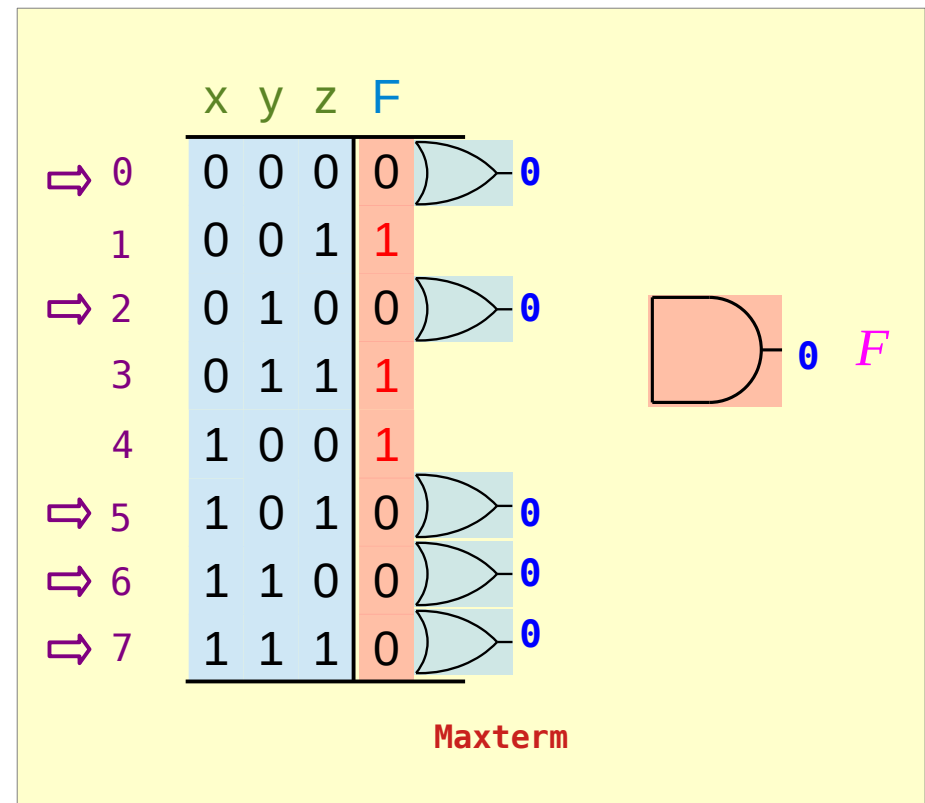
$$\begin{aligned}
 F &= m_1 + m_3 + m_4 \\
 &= \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}\bar{z}
 \end{aligned}$$



$$\begin{aligned}
 F &= M_0 + M_2 + M_5 + M_6 + M_7 \\
 &= (x+y+z) \cdot (x+\bar{y}+z) \cdot (\bar{x}+y+\bar{z}) \cdot \\
 &\quad (\bar{x}+\bar{y}+z) \cdot (\bar{x}+\bar{y}+\bar{z})
 \end{aligned}$$

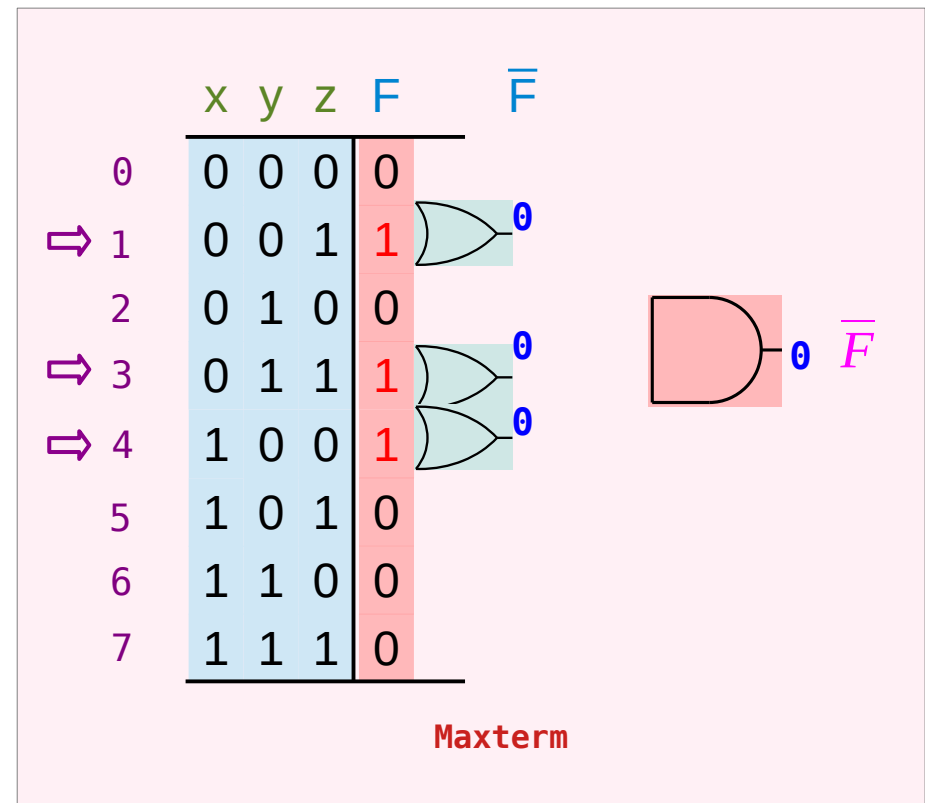
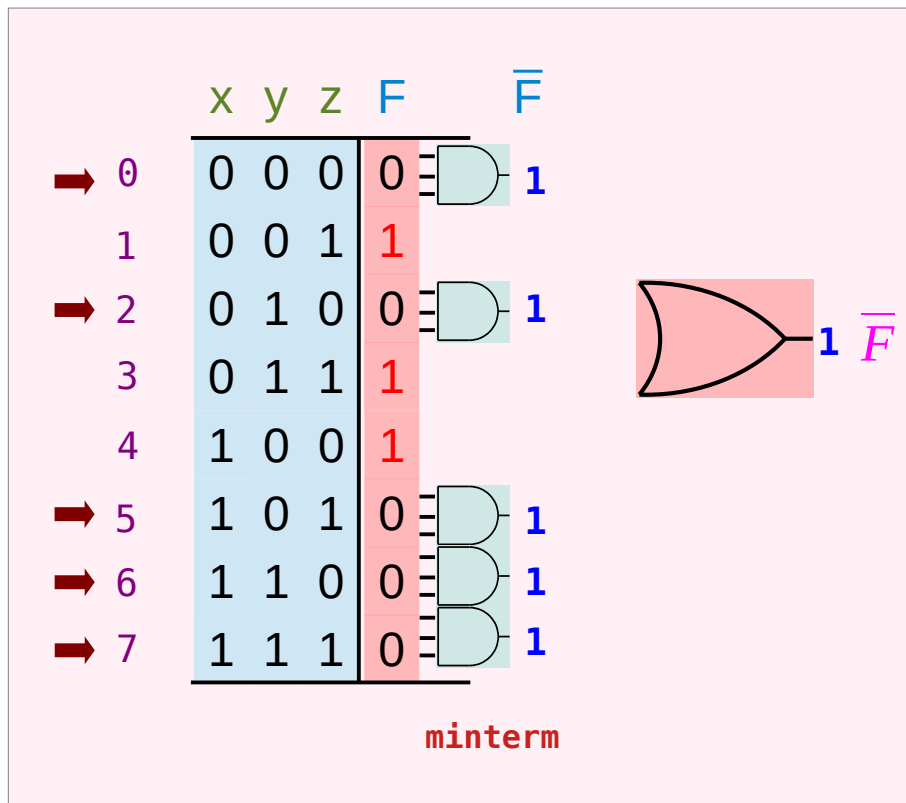
Boolean Function $\bar{F}$ with minterms and Maxterms




$$\begin{aligned}
 \bar{F} &= m_0 + m_2 + m_5 + m_6 + m_7 \\
 &= \bar{x} \cdot \bar{y} \cdot \bar{z} + \bar{x} \cdot y \cdot \bar{z} + x \cdot \bar{y} \cdot z \\
 &\quad + x \cdot y \cdot \bar{z} + x \cdot y \cdot z
 \end{aligned}$$

$$\begin{aligned}
 \bar{F} &= M_1 + M_3 + M_4 \\
 &= (x + y + \bar{z}) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{x} + y + z)
 \end{aligned}$$

SOP and POS

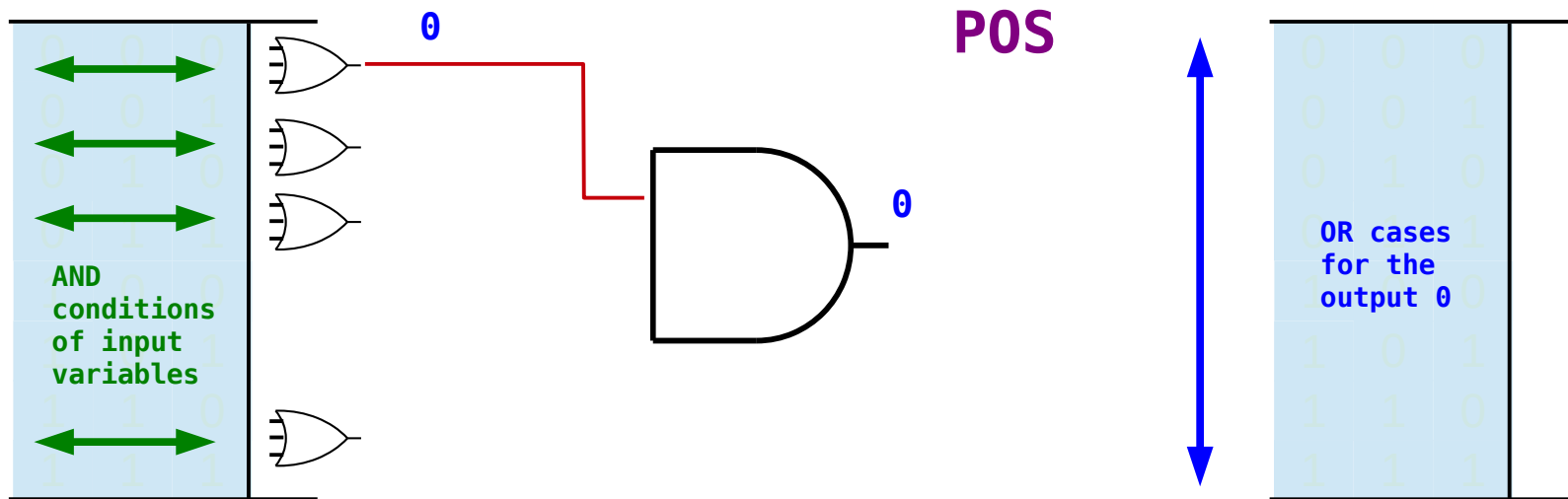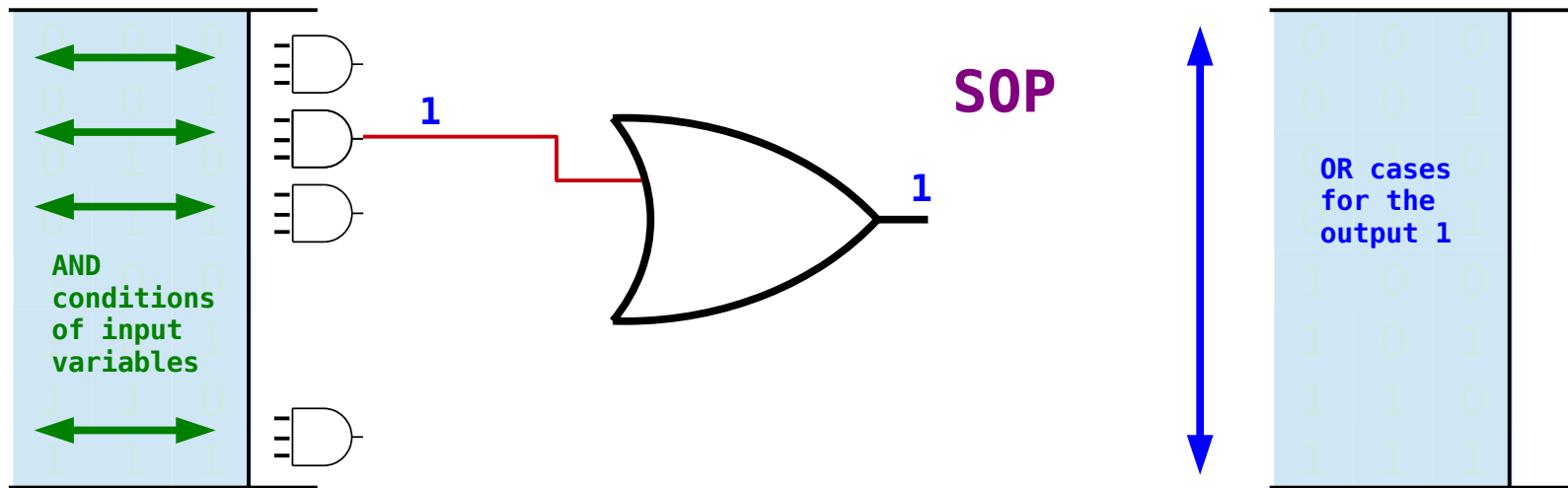


Truth Table and minterms (1)

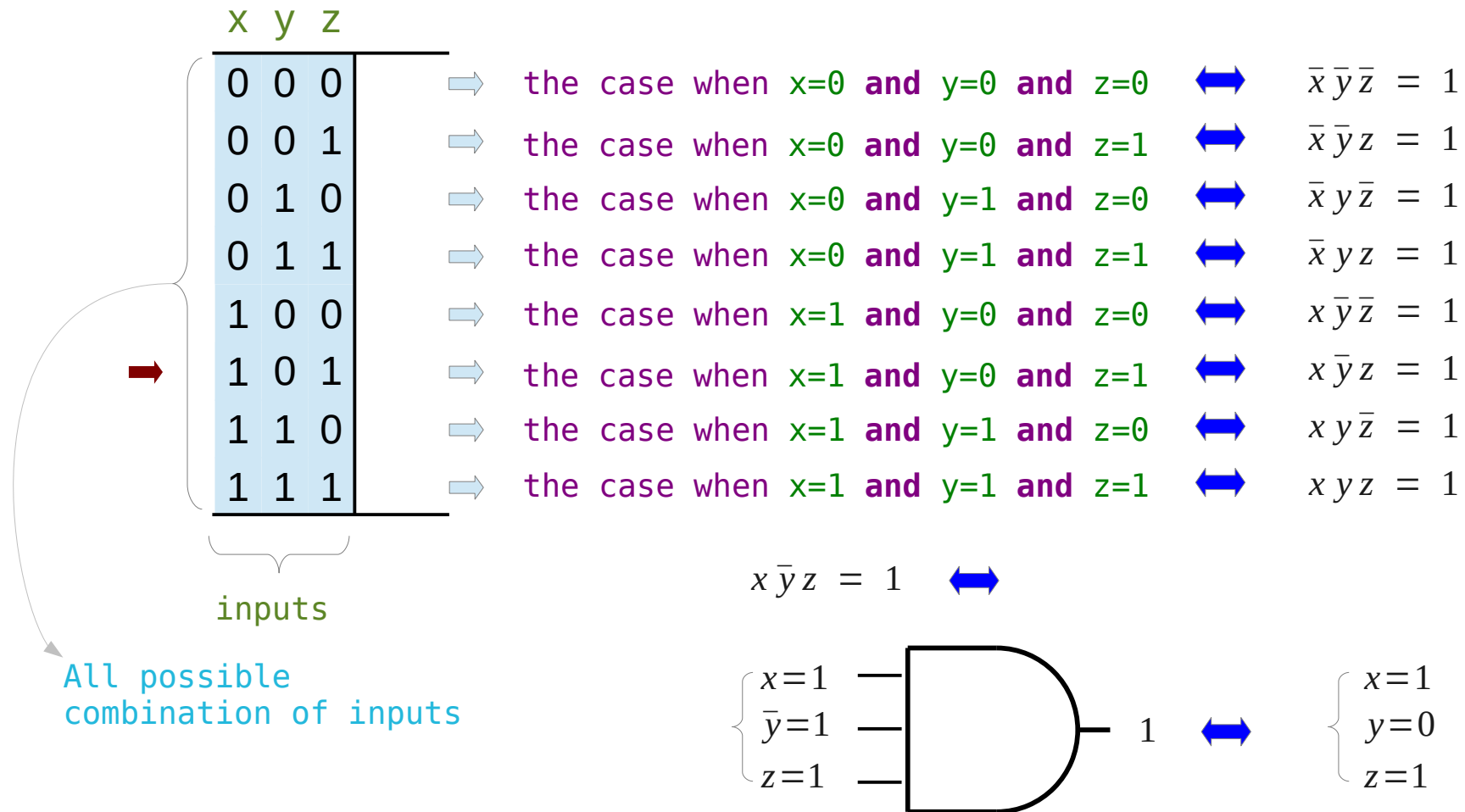

For the output of an **and** gate to be 1,
all inputs must be 1

Truth Table and MAXterms (1)

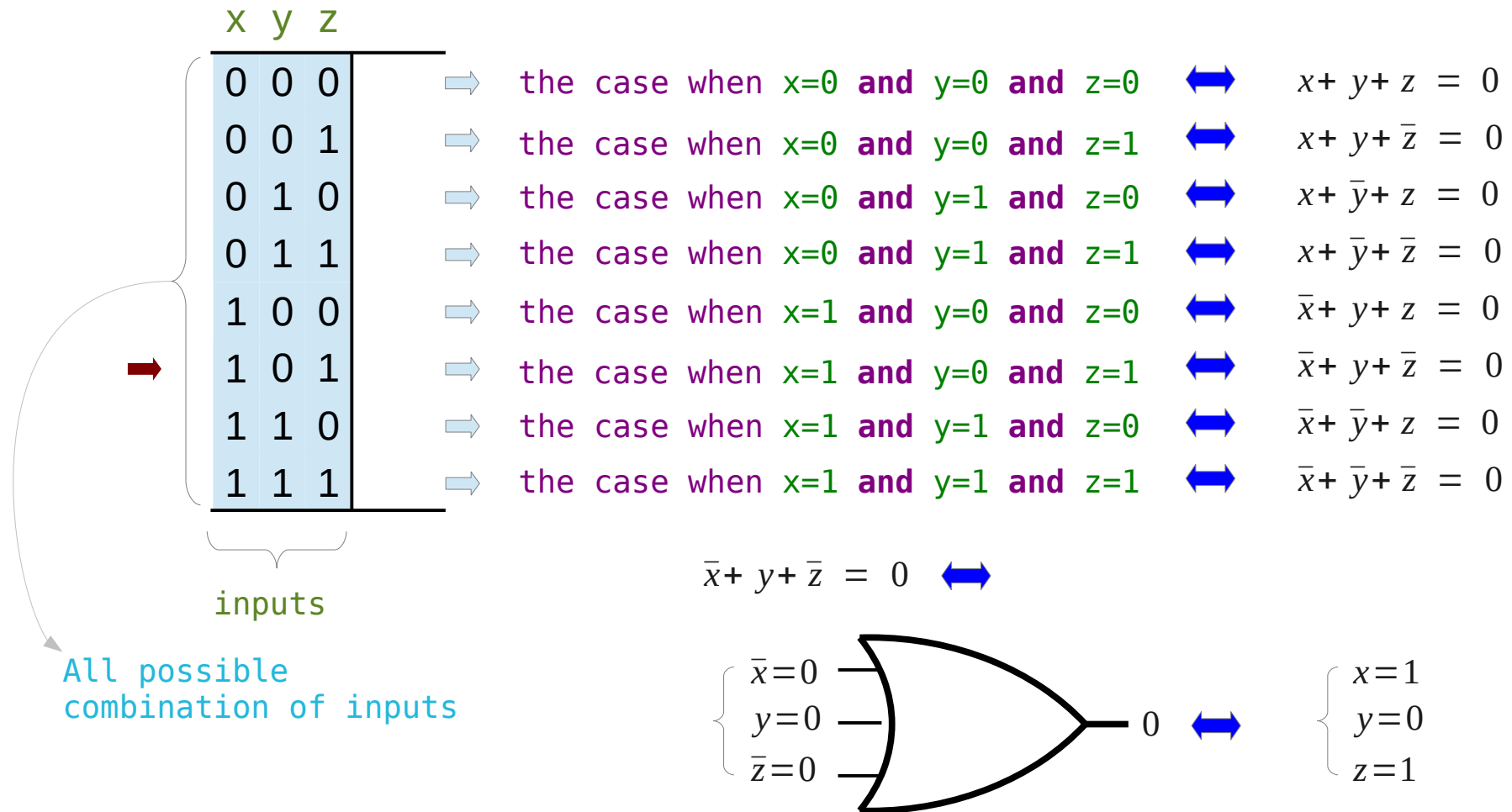

Truth Table and MAXterms (2)


	x	y	z	
0	0	0	0	→ the case when the MAXterm
1	0	0	1	→ the case when the MAXterm
2	0	1	0	→ the case when the MAXterm
3	0	1	1	→ the case when the MAXterm
4	1	0	0	→ the case when the MAXterm
→ 5	1	0	1	→ the case when the MAXterm
6	1	1	0	→ the case when the MAXterm
7	1	1	1	→ the case when the MAXterm

index







inputs

All possible combination of inputs

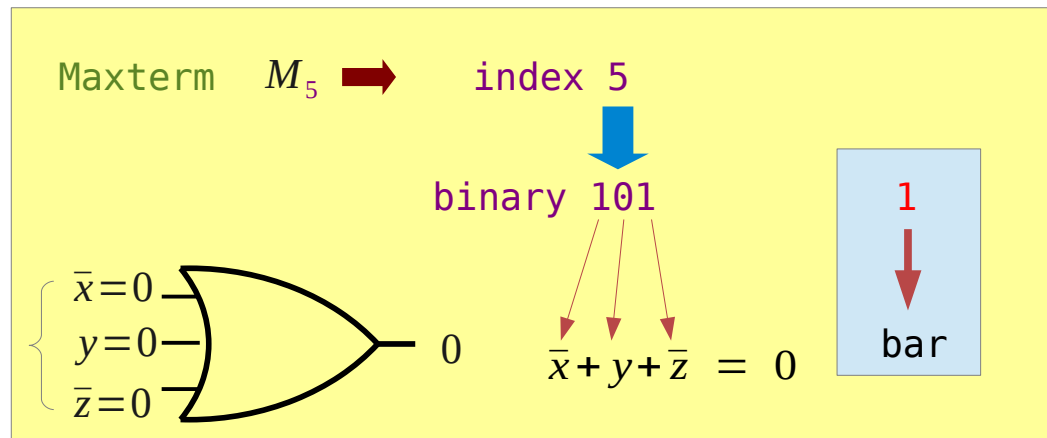$M_0 = x + y + z = 0$
 $M_1 = x + y + \bar{z} = 0$
 $M_2 = x + \bar{y} + z = 0$
 $M_3 = x + \bar{y} + \bar{z} = 0$
 $M_4 = \bar{x} + y + z = 0$
 $M_5 = \bar{x} + y + \bar{z} = 0$
 $M_6 = \bar{x} + \bar{y} + z = 0$
 $M_7 = \bar{x} + \bar{y} + \bar{z} = 0$



Maxterm and minterm Conditions

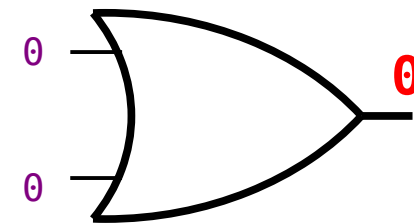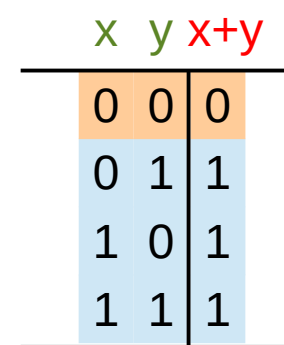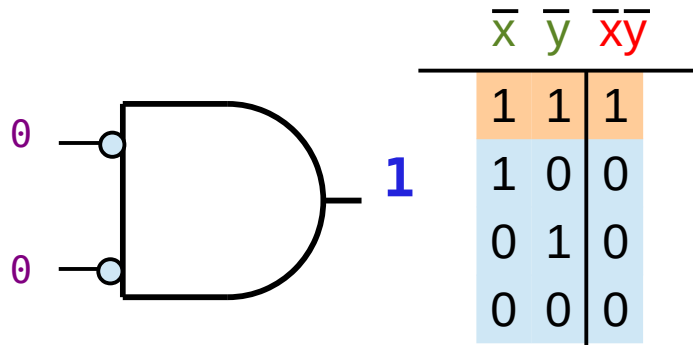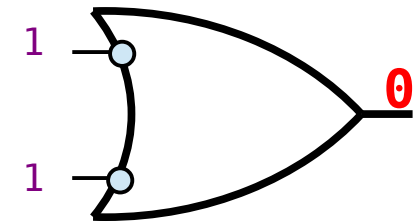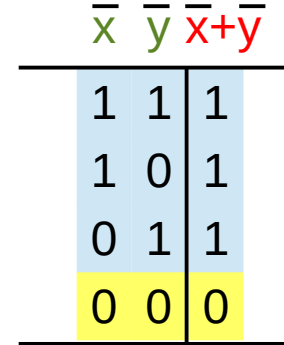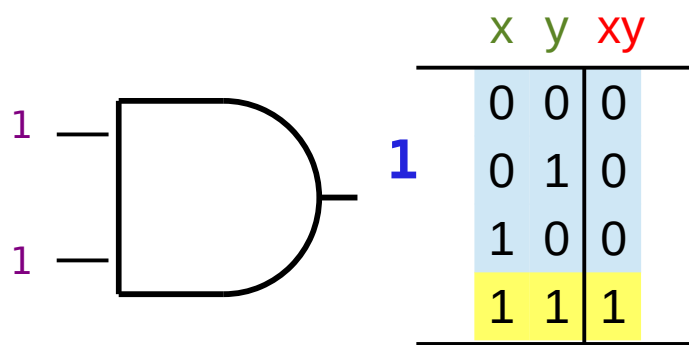

Boolean Function with minterms (1)

	x	y	z	F
0	0	0	0	0
→ 1	0	0	1	1
2	0	1	0	0
→ 3	0	1	1	1
→ 4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

index inputs output


All possible
combination of inputs

The output F becomes 1,
for one of the three following cases

(the case when $x=0$ and $y=0$ and $z=1$) $\Leftrightarrow m_1 = \bar{x}\bar{y}z = 1$

or (the case when $x=0$ and $y=1$ and $z=1$) $\Leftrightarrow m_3 = \bar{x}yz = 1$

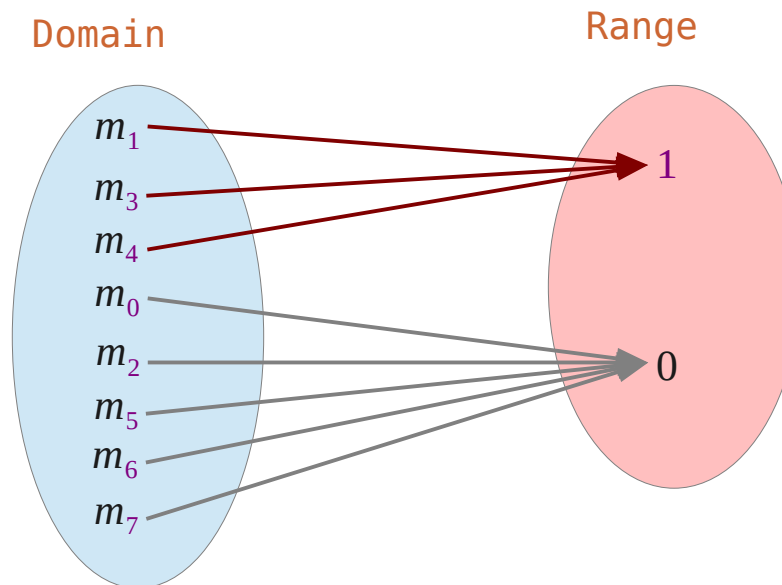or (the case when $x=1$ and $y=0$ and $z=0$) $\Leftrightarrow m_4 = x\bar{y}\bar{z} = 1$



Boolean Function with minterms (2)

	x	y	z	F
0	0	0	0	0
→ 1	0	0	1	1
2	0	1	0	0
→ 3	0	1	1	1
→ 4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0



index inputs output

All possible
combination of inputs

The output F becomes 1,
either $m_1=1$ or $m_3=1$ or $m_4=1$

$$m_1 + m_3 + m_4 = 1 \quad \Rightarrow \quad F = 1$$

$$\Leftrightarrow F = m_1 + m_3 + m_4$$

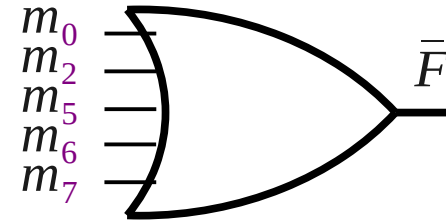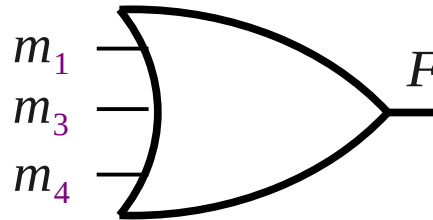

For the output of an **or** gate to be 1,
at least one must be 1

Boolean Function with minterms (3)

	x	y	z	F
0	0	0	0	0
→ 1	0	0	1	1
2	0	1	0	0
→ 3	0	1	1	1
→ 4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

index { } { }

inputs output

All possible combination of inputs

The output F becomes 1,
either $m_1=1$ or $m_3=1$ or $m_4=1$

$$m_1 + m_3 + m_4 = 1 \quad \rightleftharpoons \quad F = 1$$

$$\Leftrightarrow F = m_1 + m_3 + m_4$$

The output F becomes 0,
either $m_0=1$ or $m_2=1$ or $m_5=1$ or $m_6=1$ or $m_7=1$

$$m_0 + m_2 + m_5 + m_6 + m_7 = 1 \quad \rightleftharpoons \quad F = 0$$

$$\Leftrightarrow \bar{F} = m_0 + m_2 + m_5 + m_6 + m_7$$

For the output of an **or** gate to be 1,
at least one must be 1

Boolean Function with Maxterms (1)

The output F becomes 0,
for one of the five following cases

	x	y	z	F
→ 0	0	0	0	0
1	0	0	1	1
→ 2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
→ 5	1	0	1	0
→ 6	1	1	0	0
→ 7	1	1	1	0

index inputs output

All possible combination of inputs

(the case when $x=0$ and $y=0$ and $z=0$) $\Leftrightarrow x + y + z = 0$

or (the case when $x=0$ and $y=1$ and $z=0$) $\Leftrightarrow x + \bar{y} + z = 0$

or (the case when $x=1$ and $y=0$ and $z=1$) $\Leftrightarrow \bar{x} + y + \bar{z} = 0$

or (the case when $x=1$ and $y=1$ and $z=0$) $\Leftrightarrow \bar{x} + \bar{y} + z = 0$

or (the case when $x=1$ and $y=1$ and $z=1$) $\Leftrightarrow \bar{x} + \bar{y} + \bar{z} = 0$

Domain

Range

Boolean Function with Maxterms (2)

	x	y	z	F
→ 0	0	0	0	0
1	0	0	1	1
→ 2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
→ 5	1	0	1	0
→ 6	1	1	0	0
→ 7	1	1	1	0

index inputs output



All possible
combination of inputs

The output F becomes 0,

either $M_0=0$ or $M_2=0$ or $M_5=0$ or $M_6=0$ or $M_7=0$

$$M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 = 0 \quad \Longleftrightarrow \quad F = 0$$
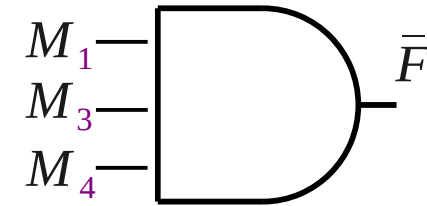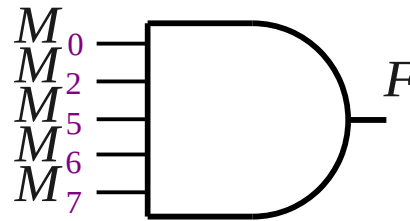
$$\Longleftrightarrow F = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7$$



For the output of an **and** gate to be 0,
at least one input must be 0

Boolean Function with Maxterms (2)

	x	y	z	F
→ 0	0	0	0	0
1	0	0	1	1
→ 2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
→ 5	1	0	1	0
→ 6	1	1	0	0
→ 7	1	1	1	0

index inputs output

All possible combination of inputs

The output F becomes 0,

either $M_0=0$ or $M_2=0$ or $M_5=0$ or $M_6=0$ or $M_7=0$

$$M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 = 0 \quad \Rightarrow \quad F = 0$$

$$\Leftrightarrow F = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7$$

The output F becomes 1,

either $M_1=0$ or $M_3=0$ or $M_4=0$

$$M_1 \cdot M_3 \cdot M_4 = 0 \quad \Rightarrow \quad F = 1$$

$$\Leftrightarrow \bar{F} = M_1 \cdot M_3 \cdot M_4$$

For the output of an **and** gate to be 0,
at least one input must be 0

Complimentary Relations

	x	y	z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

index inputs output

All possible
combination of inputs

$$m_i = \overline{M_i}$$

$$M_i = \overline{m_i}$$

$$F(x, y, z) = m_1 + m_3 + m_4$$

The output F becomes 1,
either $m_1=1$ or $m_3=1$ or $m_4=1$

For the output of an **or** gate to be 1,
at least one must be 1

$$\overline{F}(x, y, z) = m_0 + m_2 + m_5 + m_6 + m_7$$

$$\Leftrightarrow F(x, y, z) = \overline{m_0 + m_2 + m_5 + m_6 + m_7}$$

$$= \overline{m_0} \cdot \overline{m_2} \cdot \overline{m_5} \cdot \overline{m_6} \cdot \overline{m_7}$$

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7$$

The output F becomes 0,
either $M_0=0$ or $M_2=0$ or $M_5=0$ or $M_6=0$ or $M_7=0$

For the output of an **and** gate to be 0,
at least one input must be 0

Boolean Function Summary

	x	y	z	F
0	0	0	0	
1	0	0	1	1
2	0	1	0	
3	0	1	1	1
4	1	0	0	1
5	1	0	1	
6	1	1	0	
7	1	1	1	

The output F becomes 1,

for the cases

1) when $m_1=1$ or $m_3=1$ or $m_4=1$

$$F(x, y, z) = m_1 + m_3 + m_4$$

$$F=1$$

2) when $M_1=0$ or $M_3=0$ or $M_4=0$

$$\bar{F}(x, y, z) = M_1 \cdot M_3 \cdot M_4$$

$$F=1 \quad (\bar{F}=0)$$

	x	y	z	F
0	0	0	0	0
1	0	0	1	
2	0	1	0	0
3	0	1	1	
4	1	0	0	
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

The output F becomes 0,

for the cases

1) when $m_0=1$ or $m_2=1$ or $m_5=1$ or $m_6=1$ or $m_7=1$

$$\bar{F}(x, y, z) = m_0 + m_2 + m_5 + m_6 + m_7$$

$$F=0 \quad (\bar{F}=1)$$

2) when $M_0=0$ or $M_2=0$ or $M_5=0$ or $M_6=0$ or $M_7=0$

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7$$

$$F=0$$

Boolean Function Summary

	x	y	z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

	x	y	z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

$$F(x, y, z) = m_1 + m_3 + m_4 \Rightarrow F=1$$

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 \Rightarrow F=0$$

$$\overline{F}(x, y, z) = m_0 + m_2 + m_5 + m_6 + m_7 \Rightarrow F=0 \quad (\overline{F}=1)$$

$$\overline{F}(x, y, z) = M_1 \cdot M_3 \cdot M_4 \Rightarrow F=1 \quad (\overline{F}=0)$$

Truth Table

References

[1] <http://en.wikipedia.org/>