

Noise Margin (C1)

Copyright (c) 2025-2011 Young W. Lim.


Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Fan-in and Fan-out


fan-in = 2

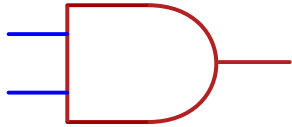


fan-in = 3




fan-in = 4

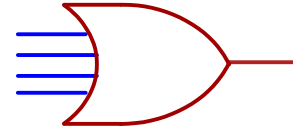


fan-out = 2

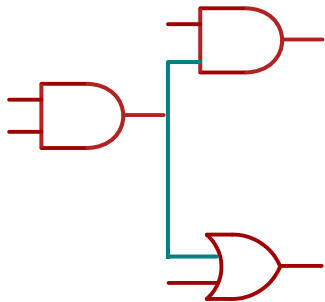

fan-out = 3

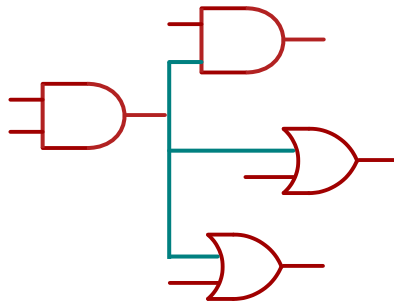


fan-out = 4

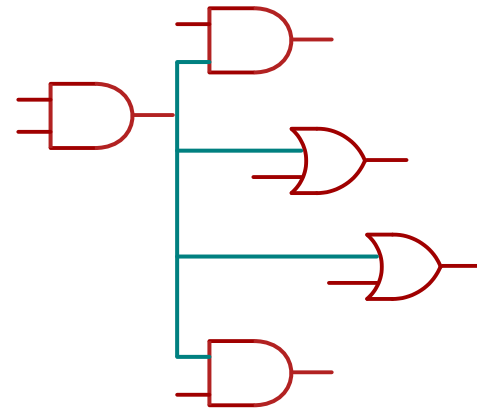

Fan-in and Fan-out


higher fan-in $\leftarrow$ complex logic functions

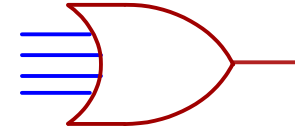- with fewer gates
- complicated circuit design
- increase propagation delay






manage fan-out $\rightarrow$ maintain circuit integrity

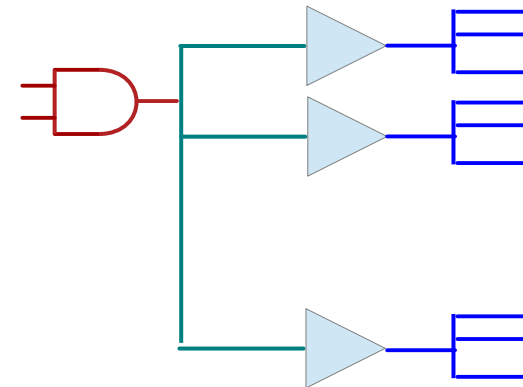- reliable transmission
- without significant degradation



High State Noise Margin

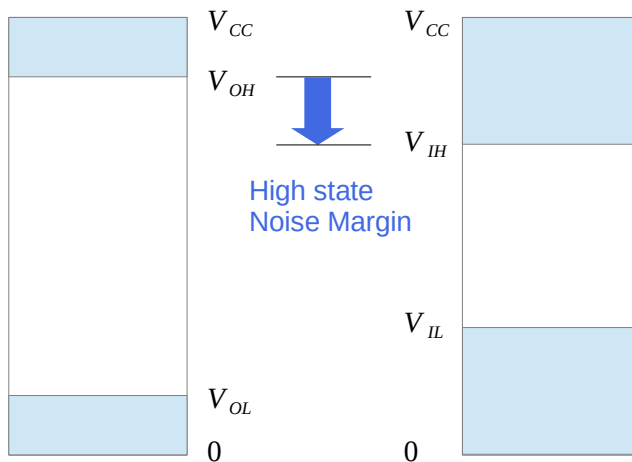
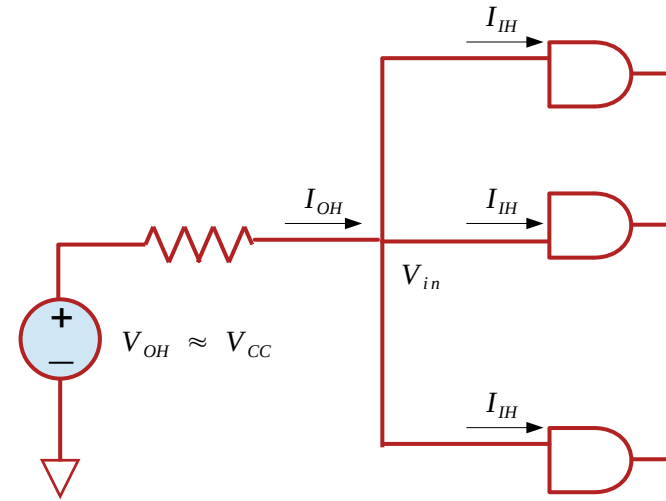
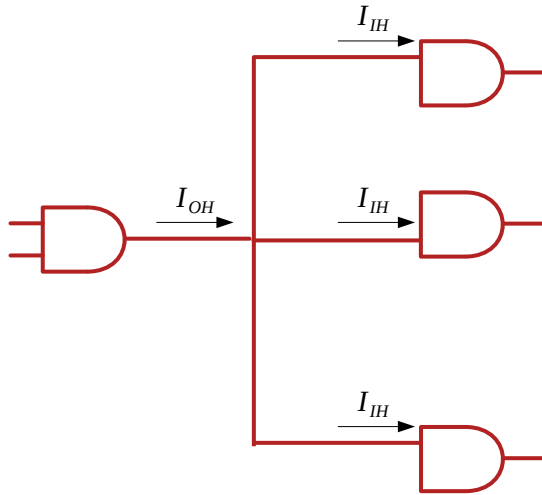


$$V_{in} = V_{OH} - n \cdot I_{IH} > V_{IH}$$

to detect the input as logic '1',
the fan-out gate should receive a
voltage greater than V_{IH} .

But as n increases V_{in} decreases

Low State Noise Margin

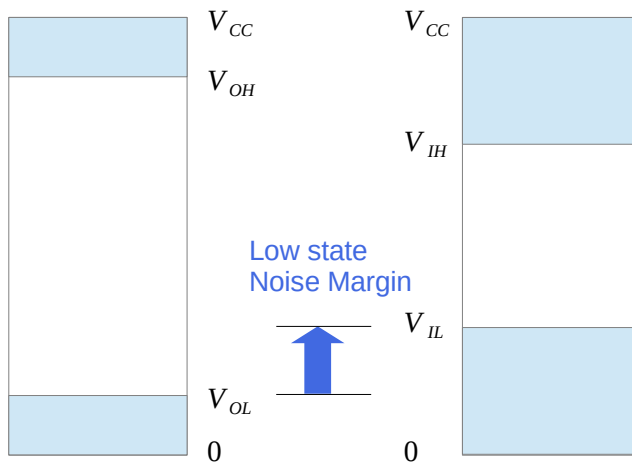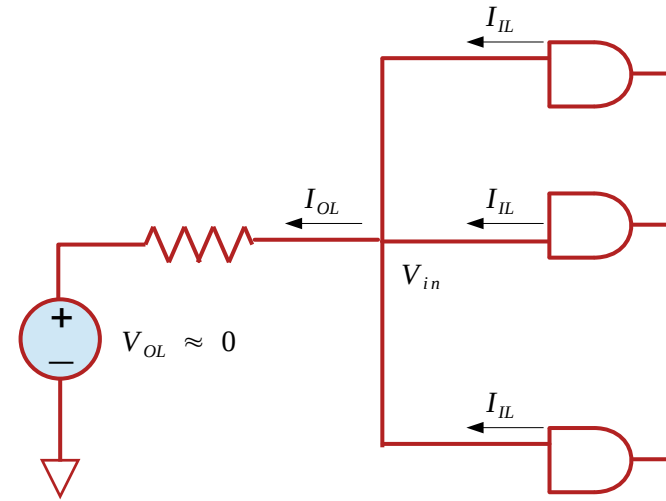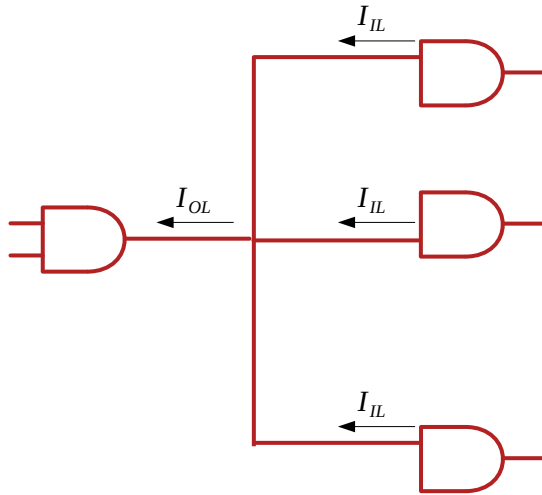

$$V_{in} = V_{OL} + n \cdot I_{IL} < V_{IL}$$

to detect the input as logic '0',
the fan-out gate should receive a
voltage less than V_{IL} .

But as n increases V_{in} increases

Fan-in and Fan-out


A quantitative measure of noise immunity

the higher the noise margin, the more robust the circuit

the high-state and low-state **noise margins** as follows:

High-State Noise Margin (V_{NH}): $V_{OH(min)} - V_{IH(min)}$

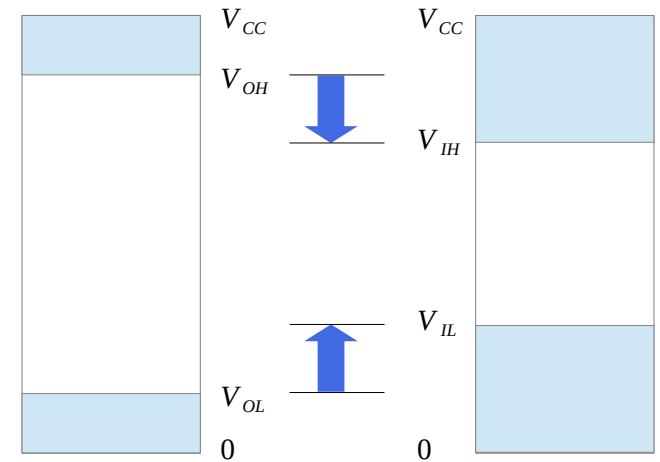Low-State Noise Margin (V_{NL}): $V_{IL(max)} - V_{OL(max)}$



$V_{OH(min)}$ = **minimum** output voltage in the High state.

$V_{OL(max)}$ = **maximum** output voltage in the Low state.

$V_{IH(min)}$ = **minimum** input voltage required to be recognized as a High state.

$V_{IL(max)}$ = **maximum** input voltage allowed to be recognized as a Low state.

<https://www.rfwireless-world.com/terminology/rf-components/fanout-vs-noise-margin>

Fan-in and Fan-out

calculating Fanout are:

Fanout (High): $I_{OH(max)} / I_{IH(max)}$

Fanout (Low): $I_{OL(max)} / I_{IL(max)}$

$I_{OH(max)}$ = maximum output current in the High state.

$I_{OL(max)}$ = maximum output current in the Low state.

$I_{IH(max)}$ = maximum input current required to maintain a High state.

$I_{IL(max)}$ = maximum input current required to maintain a Low state.


the overall Fanout is the lower value between Fanout (High) and Fanout (Low).

this ensures that the gate can reliably drive the specified number of loads in both the high and low states.

<https://www.rfwireless-world.com/terminology/rf-components/fanout-vs-noise-margin>

increasing current →
increasing voltage drop

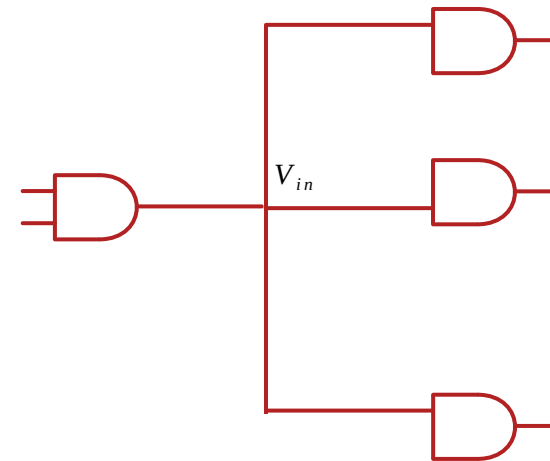decreasing $V_{in,H}$
increasing $V_{in,L}$



Truth Table

References

[1] <http://en.wikipedia.org/>