

Carry Lookahead Adder (2A)

-
-

Copyright (c) 2025 - 2013 Young W. Lim.


Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


Carry Kill, Propagate, Generate conditions (1)

X	Y		
0	0	K	Kill ($=\overline{P}G$)
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

 


<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>

 Carry Kill, Propagate, Generate conditions (2)



K, P, and G conditions in a 2-bit adder (1)

X	Y		
0	0	K	Kill ($=\bar{P}\bar{G}$)
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

 

Unless the two FA's are in **propagate** mode, the transition of **Cin** does not affect the transition of **Cout**


Critical path – all FA's in **propagate** mode

Broken paths for any FA in other mode
- kill mode, **generate** mode

<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>


K, P, and G conditions in a 2-bit adder (2)

X	Y		
0	0	K	Kill ($=\bar{P}G$)
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

 


K	K	0
K	K	1
K	P	0
K	P	1
K	G	0
K	G	1
P	K	0
P	K	1
P	P	0
P	P	1
P	G	0
P	G	1
G	K	0
G	K	1
G	P	0
G	P	1
G	G	0
G	G	1

 
1. Cases when **FA1** is in the **K** mode



 
2. Cases when **FA1** is in the **P** mode



 
3. Cases when **FA1** is in the **G** mode




Cases for $C_{out} = 1$

 

Cases for $C_{out} = 0$

 


FA with P & G

 

Half Adder	
S	$= a \oplus b$
C	$= a \wedge b$

a	b	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Full adder with additional generate and propagate signals.

https://en.wikipedia.org/wiki/Carry-skip_adder

Ripple Carry Adder


$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$

$$\begin{aligned} c_1 &= g_0 + p_0 \wedge c_0 \\ c_2 &= g_1 + p_1 \wedge c_1 \\ c_3 &= g_2 + p_2 \wedge c_2 \\ c_4 &= g_3 + p_3 \wedge c_3 \end{aligned}$$


generated carry

propagated carry

 

https://en.wikipedia.org/wiki/Carry-skip_adder

4-bit Full Adder with P and G

 

Half Adder

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$


Half Adder

$$c_{i+1} = g_i + p_i \wedge c_i$$

$$s_i = p_i \oplus c_i$$


<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

C_0 propagation condition

 


c_0 can be propagated to c_{out} only when $s = 1$
 
$$\begin{aligned}
 s &= p_3 \wedge p_2 \wedge p_1 \wedge p_0 = p_{[3:0]} \\
 &= (a_3 \oplus b_3) \\
 &\quad \wedge (a_2 \oplus b_2) \\
 &\quad \wedge (a_1 \oplus b_1) \\
 &\quad \wedge (a_0 \oplus b_0)
 \end{aligned}$$



https://en.wikipedia.org/wiki/Carry-skip_adder

Propagated and Generated Carries

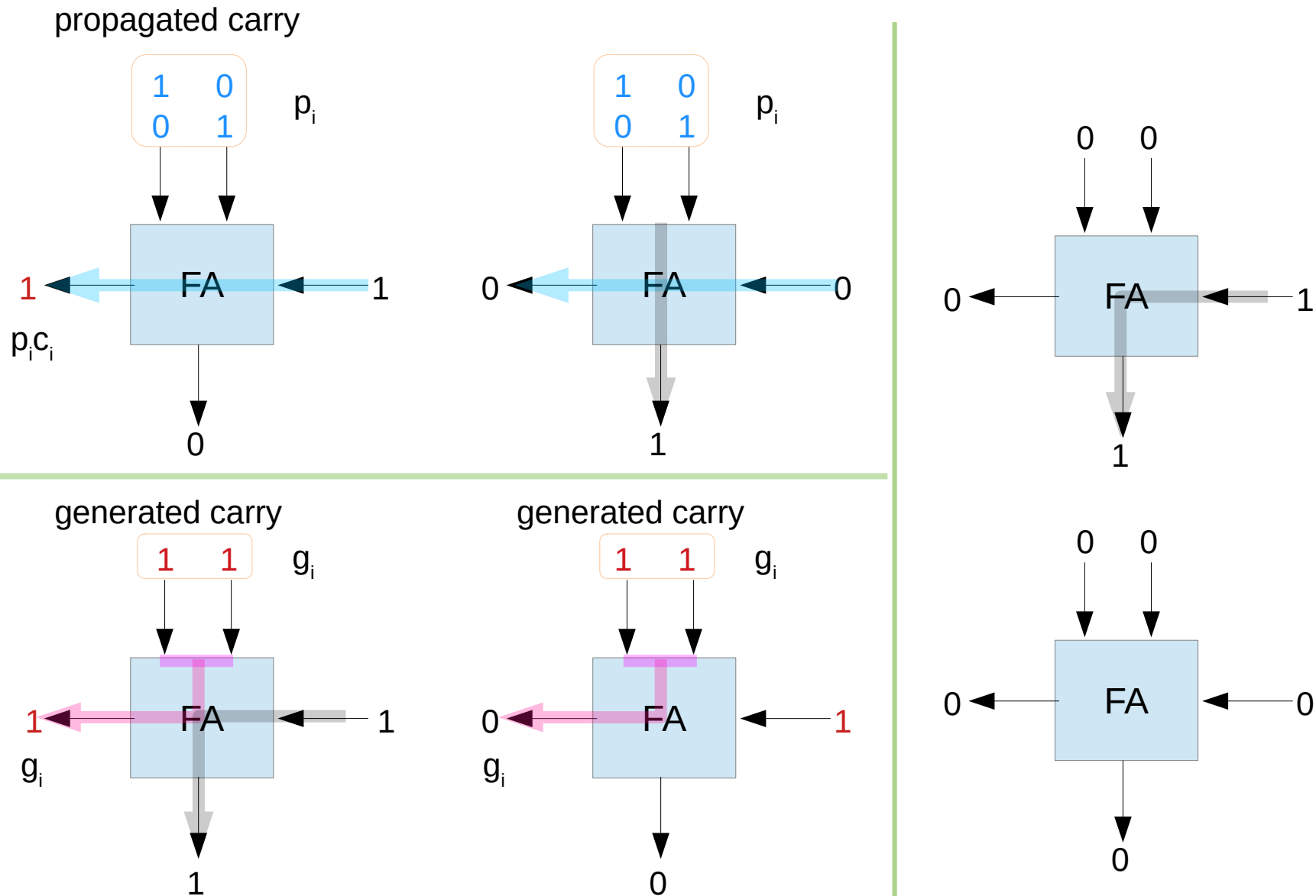

Invert

Invert

$$(C1_3 \oplus C1_2)$$

$$\begin{array}{cc} P & P \\ G & G \end{array}$$


$$C1 = X + Y$$

$$C0 = X \cdot Y$$


$$C1 \oplus C0 = X \oplus Y = P$$

$$\begin{array}{cc} P & G \\ G & \end{array}$$

 
$$\begin{array}{cc} P & P'G' \\ G & P'G' \\ \hline P'G' & P \\ P'G' & G \end{array}$$





Variable Block

 

Variable Block



 


Propagate

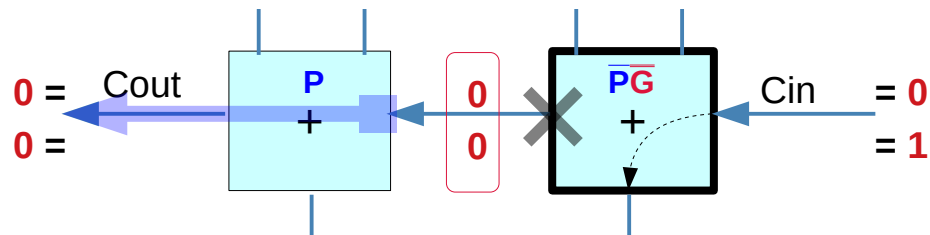 


Invert

Variable Block

   


Invert


Variable Block

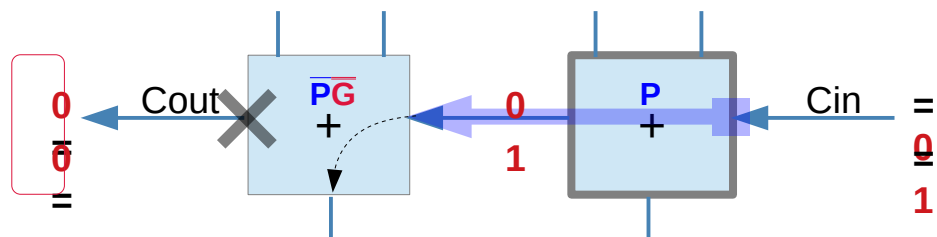


Invert

 



Invert

 


Variable Block

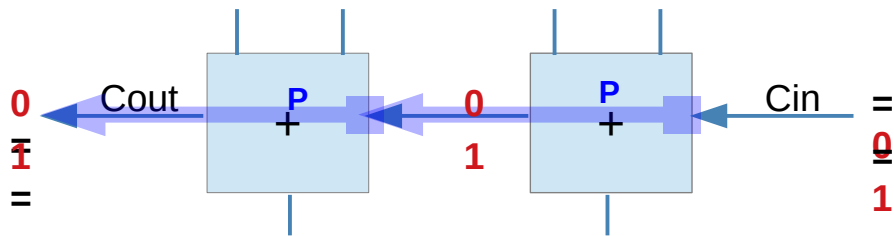

Propagate

 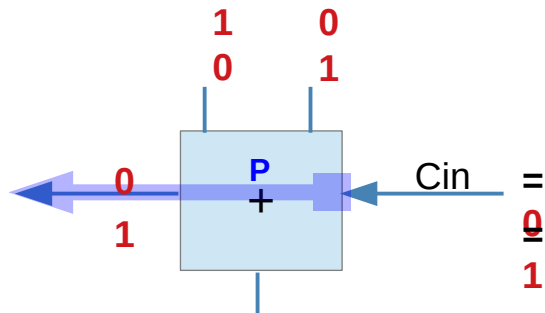


Carry Lookahead Adder

 

Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al


Carry Lookahead Adder

 

$$\begin{aligned}
 G_0 + P_0 c_0 &= c_1 \\
 G_1 + P_1 G_0 + P_1 P_0 c_0 &= c_2 \\
 G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0 &= c_3 \\
 G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0 &= c_4
 \end{aligned}$$


Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

FA with P & G

 

Half Adder	
$S = a \oplus b$	
$C = a \wedge b$	


a	b	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Full adder with additional generate and propagate signals.

https://en.wikipedia.org/wiki/Carry-skip_adder

4-bit Full Adder with P and G

 

Half Adder

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$


Half Adder

$$c_{i+1} = g_i + p_i \wedge c_i$$


$$s_i = p_i \oplus c_i$$

<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

4-bit Full Adder with P and G

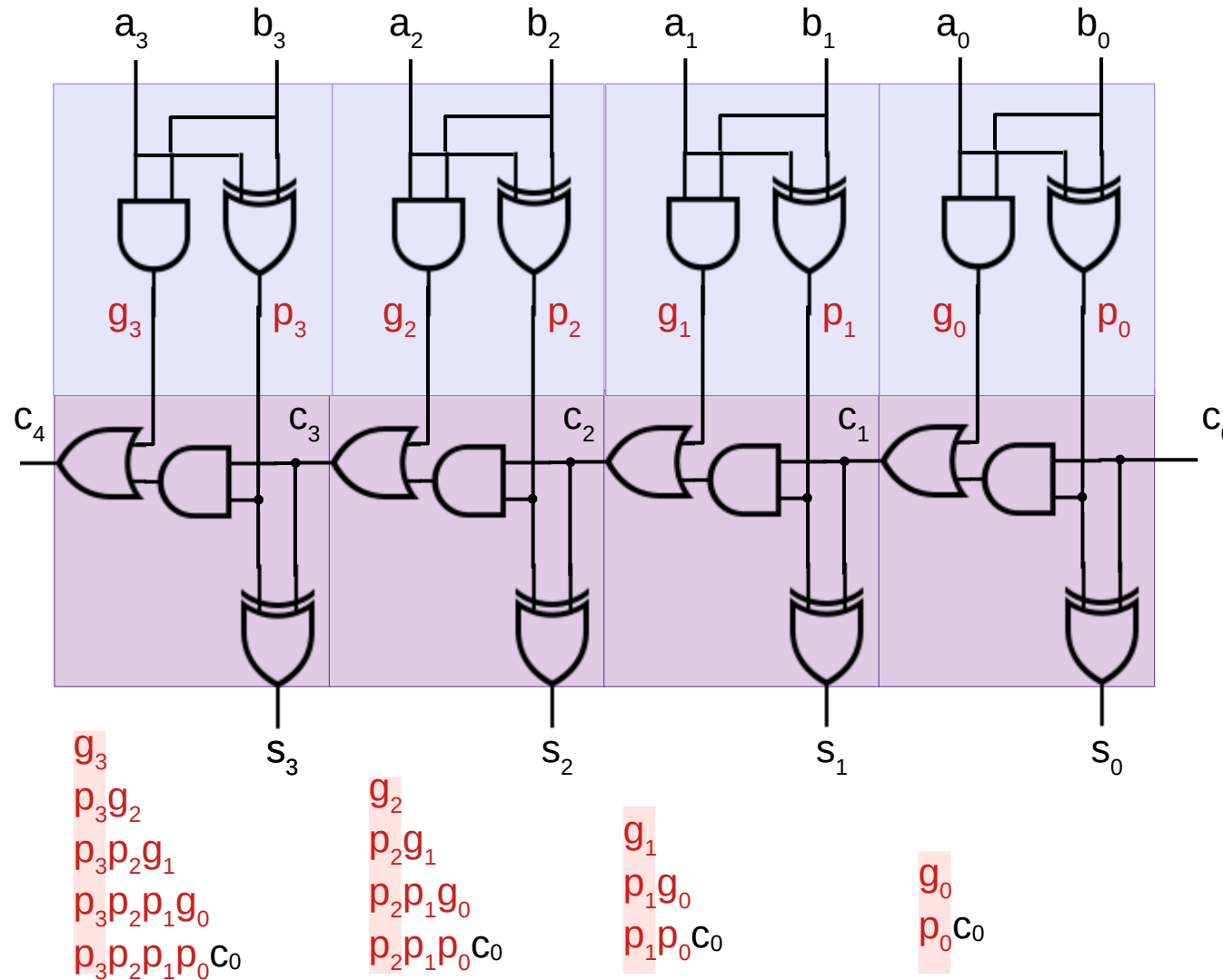

4-bit Full Adder with P and G

 



Carry Equations into Gates (2)

$$G_0 + P_0 c_0 = c_1$$


$$G_1 + P_1 G_0 + P_1 P_0 c_0 = c_2$$

$$G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0 = c_3$$
  
$$G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0 = c_4$$



Fan-in number: large
Stage number: small

 

Carry Equations

$$c_{i+1} = G_i + P_i c_i$$

$$c_1 = G_0 + P_0 c_0$$

$$c_1 = G_0 + P_0 c_0$$

$$c_2 = G_1 + P_1 c_1$$

$$c_2 = G_1 + P_1 [G_0 + P_0 c_0]$$

$$c_3 = G_2 + P_2 c_2$$

$$c_3 = G_2 + P_2 [G_1 + P_1 [G_0 + P_0 c_0]]$$

$$c_4 = G_3 + P_3 c_3$$

$$c_4 = G_3 + P_3 [G_2 + P_2 [G_1 + P_1 [G_0 + P_0 c_0]]]$$

$$G_0 + P_0 c_0 = c_1$$

$$G_1 + P_1 G_0 + P_1 P_0 c_0 = c_2$$

$$G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0 = c_3$$

$$G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0 = c_4$$

Carry Equations into Gates (1)

$$c_{i+1} = G_i + P_i c_i$$

$$c_1 = G_0 + P_0 c_0$$

$$c_2 = G_1 + P_1 c_1$$

$$c_3 = G_2 + P_2 c_2$$

$$c_4 = G_3 + P_3 c_3$$


$$c_1 = G_0 + P_0 c_0$$

$$c_2 = G_1 + P_1 [G_0 + P_0 c_0]$$

$$c_3 = G_2 + P_2 [G_1 + P_1 [G_0 + P_0 c_0]]$$

$$c_4 = G_3 + P_3 [G_2 + P_2 [G_1 + P_1 [G_0 + P_0 c_0]]]$$

Fan-in number: small
Stage number: large

 

Full Carry Lookahead

AND2, OR2	$G_0 + P_0 c_0 = c_1$
AND3, OR3	$G_1 + P_1 G_0 + P_1 P_0 c_0 = c_2$
AND4, OR4	$G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0 = c_3$
AND5, OR5	$G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0 = c_4$
AND32, OR32	$= c_{31}$
AND33, OR33	$= c_{32}$

Large number of fan-in : Impractical

{ High Radix Addition (2^g)
Multi-level Lookahead


4-bit Carry Lookahead Logic – interface

All G_i 's P_i 's are computed
simultaneously from a_i and b_i

each c_i 's takes 2 gate delays

$$G_i = a_i \cdot b_i$$

$$P_i = a_i \oplus b_i$$

 


4-bit Carry Lookahead Logic – boolean equations

All G_i 's P_i 's are computed simultaneously from a_i and b_i

each c_i 's takes 2 gate delays

$$G_i = a_i \cdot b_i$$

$$P_i = a_i \oplus b_i$$

 


4-bit Carry Lookahead Logic – POS

All G_i 's P_i 's are computed
simultaneously from a_i and b_i


each c_i 's takes 2 gate delays

$$G_i = a_i \cdot b_i$$


$$P_i = a_i \oplus b_i$$

 

4-bit CLA

 


Multi-level Carry Lookahead

 


{ High Radix Addition (2^g)
Multi-level Lookahead


Multi-level Carry Lookahead

 

Contiguous Multi-level Carry Lookahead

 

Group Carry Lookahead Logic

 

GG and PG (1)

$$c_1 = G_0 + P_0 c_0$$

$$c_2 = G_1 + P_1 [G_0 + P_0 c_0]$$

$$c_3 = G_2 + P_2 [G_1 + P_1 [G_0 + P_0 c_0]]$$

$$c_4 = G_3 + P_3 [G_2 + P_2 [G_1 + P_1 [G_0 + P_0 c_0]]]$$

$$c_4 = \boxed{G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0} + \boxed{P_3 P_2 P_1 P_0} c_0 = \boxed{GG_0} + \boxed{PG_0} c_0$$

$$c_5 = G_4 + P_4 [c_4]$$

$$c_6 = G_5 + P_5 [G_4 + P_4 [c_4]]$$

$$c_7 = G_6 + P_6 [G_5 + P_5 [G_4 + P_4 [c_4]]]$$

$$c_8 = G_7 + P_7 [G_6 + P_6 [G_5 + P_5 [G_4 + P_4 [c_4]]]]$$

$$c_8 = \boxed{G_7 + P_7 G_6 + P_7 P_6 G_5 + P_7 P_6 P_5 G_4} + \boxed{P_7 P_6 P_5 P_4} c_4 = \boxed{GG_1} + \boxed{PG_1} c_4$$

GG and PG (2)

$$c_9 = G_8 + P_8[c_8]$$

$$c_{10} = G_9 + P_9[G_8 + P_8[c_8]]$$

$$c_{11} = G_{10} + P_{10}[G_9 + P_9[G_8 + P_8[c_8]]]$$

$$c_{12} = G_{11} + P_{11}[G_{10} + P_{10}[G_9 + P_9[G_8 + P_8[c_8]]]]$$

$$c_{12} = [G_{11} + P_{11}G_{10} + P_{11}P_{10}G_9 + P_{11}P_{10}P_9G_8] + [P_{11}P_{10}P_9P_8]c_8 = [GG_2] + [PG_2]c_8$$

$$c_{13} = G_{12} + P_{12}[c_{12}]$$

$$c_{14} = G_{13} + P_{13}[G_{12} + P_{12}[c_{12}]]$$

$$c_{15} = G_{15} + P_{15}[G_{13} + P_{13}[G_{12} + P_{12}[c_{12}]]]$$

$$c_{16} = G_{16} + P_{16}[G_{15} + P_{15}[G_{13} + P_{13}[G_{12} + P_{12}[c_{12}]]]]$$

$$c_{16} = [G_{16} + P_{16}G_{15} + P_{16}P_{15}G_{14} + P_{16}P_{15}P_{14}G_{13}] + [P_{16}P_{15}P_{14}P_{13}]c_0 = [GG_3] + [PG_3]c_{12}$$


Critical Path in the Carry Lookahead Logic

All G_i 's P_i 's are computed simultaneously from a_i and b_i


each c_i 's takes 2 gate delays

$$G_i = a_i \cdot b_i$$


$$P_i = a_i \oplus b_i$$

 


Critical Path in the 4-bit CLA

 

 Critical Path in the Group Carry Lookahead Logic



Carry Skip Adder

 

Any kill or generate condition results in divided (broken) critical paths

All FA's in R-2 groups must have the propagate condition